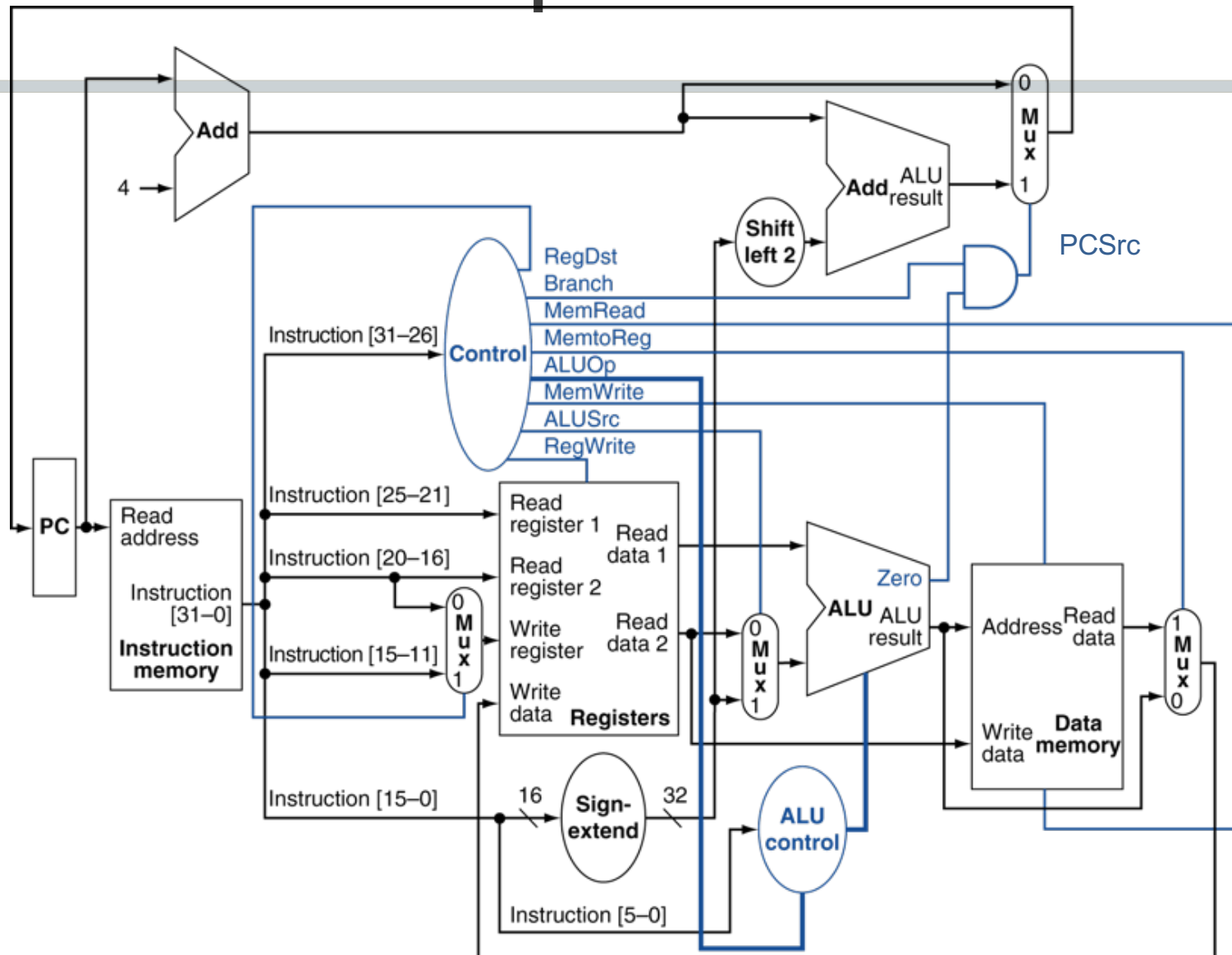



# RoadMap

- 1. Analyze instruction set  $\Rightarrow$  datapath requirements ✓
- 2. Select set of datapath components and establish clocking methodology ✓
- 3. Assemble datapath meeting the requirements ✓
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer ←
- 5. Assemble the control logic

# Review: Datapath w/ Control



# Review: Main Control

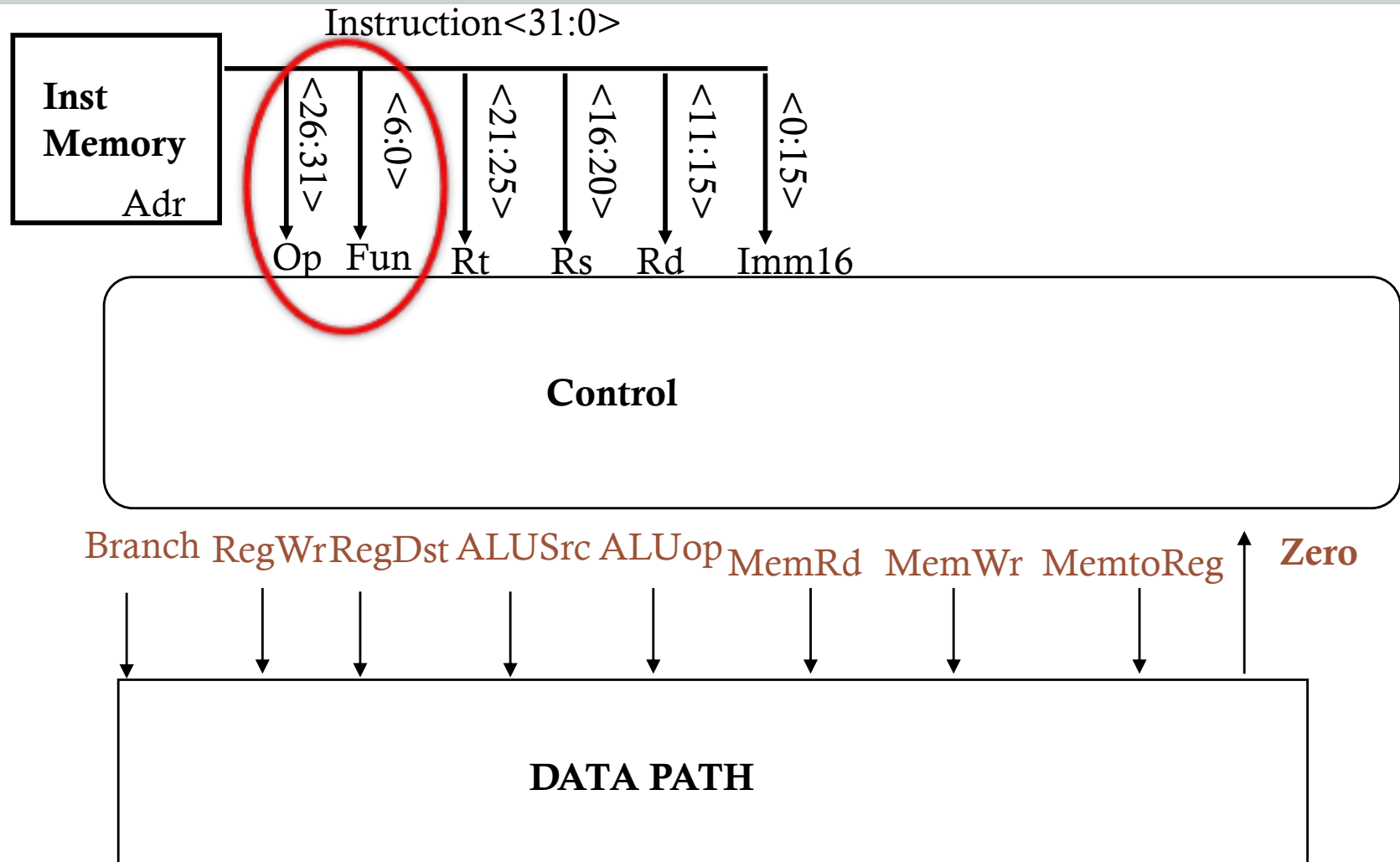

# Design the Main Control Unit

- Seven control signals in addition to ALUOp

RegWrite

MemRead

MemWrite

All derived from 6-bit Opcode

RegDst \*

ALUSrc \*

MemtoReg \*


Branch(PCSrc\*)

\* is to a mux


# Control Signals

1.  $\text{RegDst} = 0 \Rightarrow$  Register destination number for the Write register comes from the  $\text{rt}$  field (bits 20-16)  
 $\text{RegDst} = 1 \Rightarrow$  Register destination number for the Write register comes from the  $\text{rd}$  field (bits 15-11)
2.  $\text{RegWrite} = 1 \Rightarrow$  The register on the Write register input is written with the data on the Write data input (at the next clock edge)
3.  $\text{ALUSrc} = 0 \Rightarrow$  The second ALU operand comes from Read data 2  
 $\text{ALUSrc} = 1 \Rightarrow$  The second ALU operand comes from the sign-extension unit
4.  $\text{Branch} = 1 \Rightarrow$  branch instruction;  $\text{PCSrc} = 0 \Rightarrow$  The PC is replaced with  $\text{PC}+4$   
 $\text{PCSrc} = 1 \Rightarrow$  The PC is replaced with the branch target address
5.  $\text{MemtoReg} = 0 \Rightarrow$  The value fed to the register write data input comes from the ALU  
 $\text{MemtoReg} = 1 \Rightarrow$  The value fed to the register write data input comes from the data memory
6.  $\text{MemRead} = 1 \Rightarrow$  Read data memory
7.  $\text{MemWrite} = 1 \Rightarrow$  Write data memory

# Datapath With Control

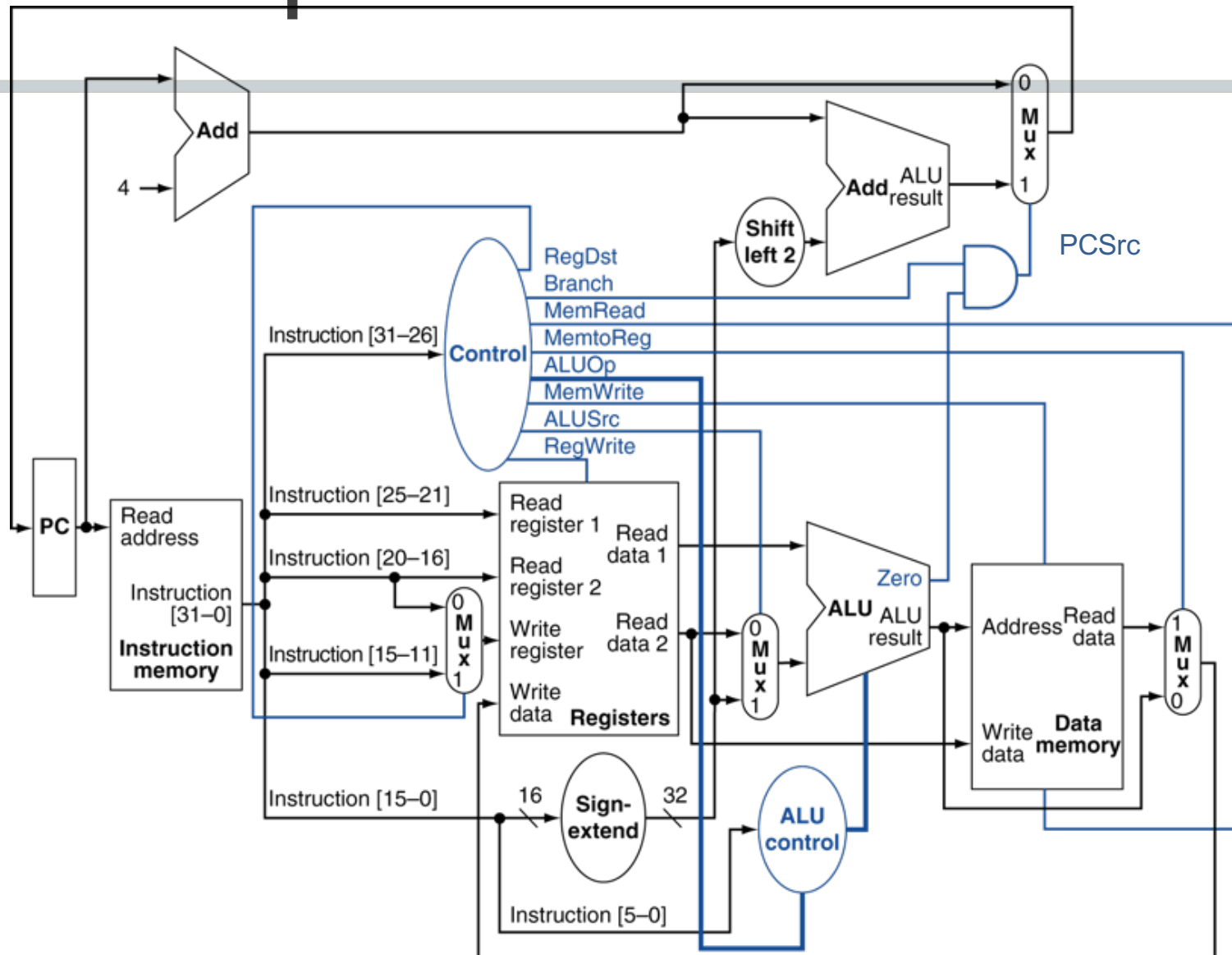

# R-Type Instruction

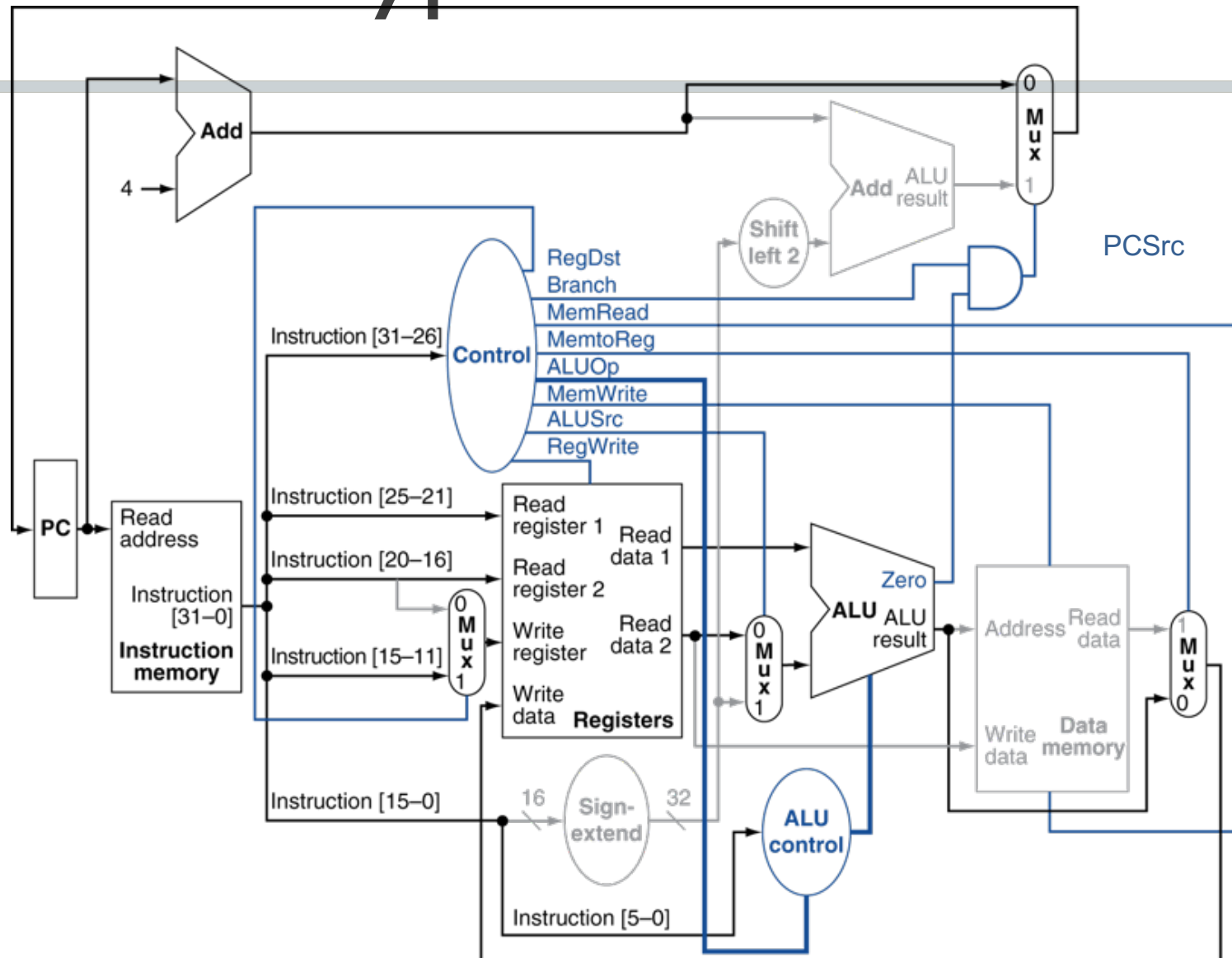

# R-format Instructions

ALUOp = 10

MemRead = 0

MemWrite = 0

RegWrite = 1

Branch = 0


RegDst = 1

ALUSrc = 0

MemtoReg = 0



# Load Instruction

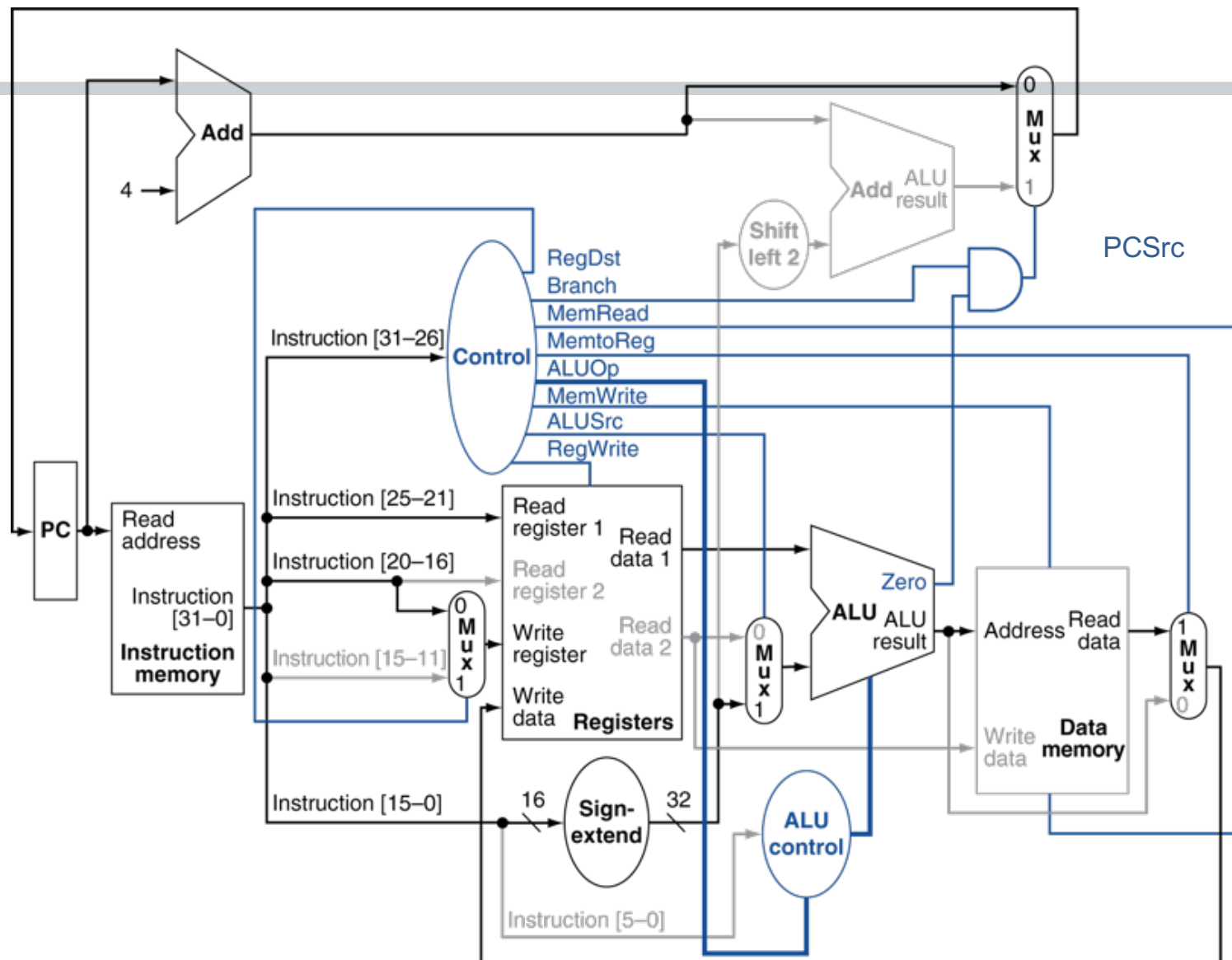

# Memory Access Instructions

Load word

Store Word?

ALUOp = 00

MemRead = 1

MemWrite = 0

RegWrite = 1


Branch = 0

RegDst = 0

ALUSrc = 1

MemtoReg = 1

# Branch-on-Equal Instruction

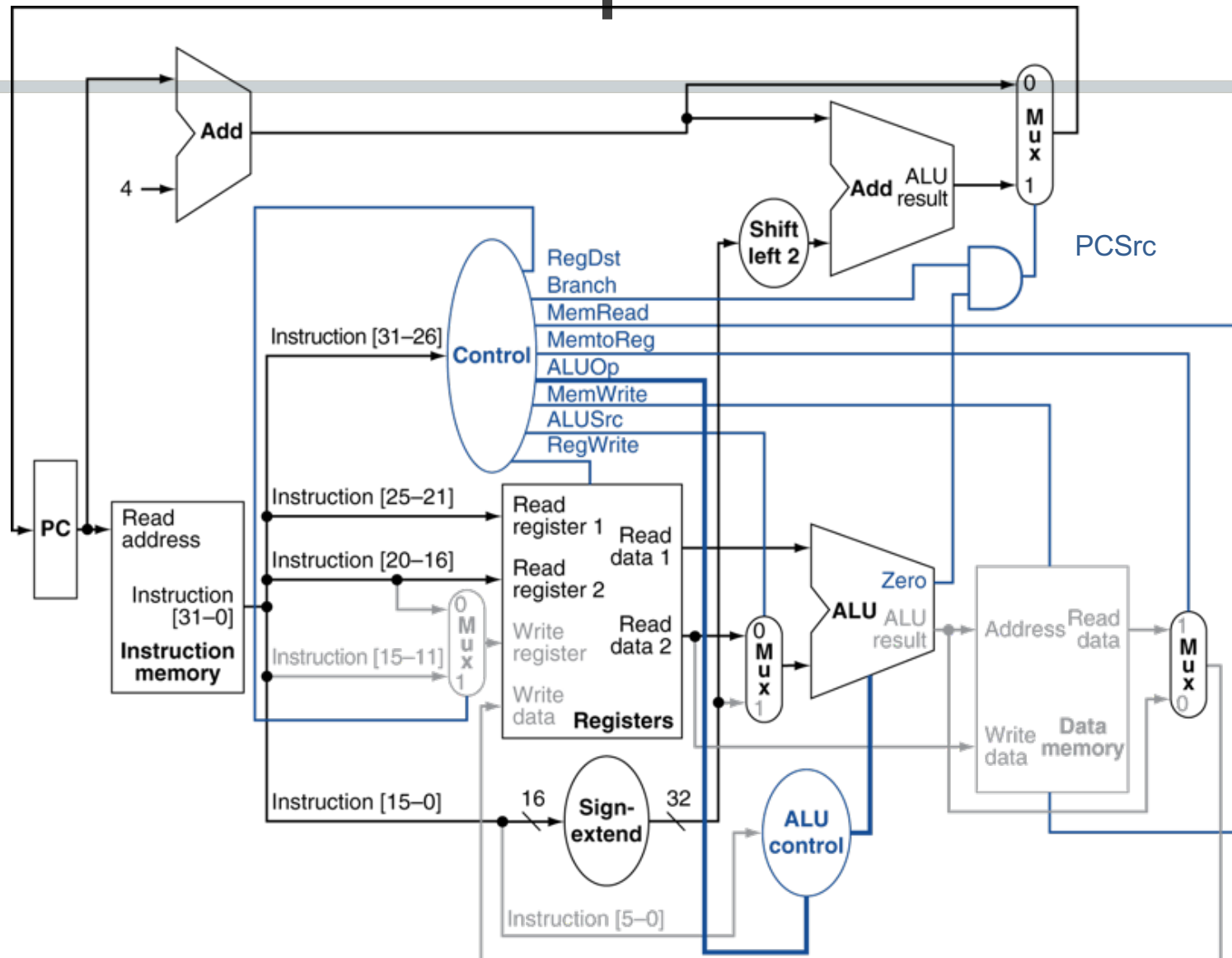

# Branch on Equal

ALUOp = 01

MemRead = 0

MemWrite = 0

RegWrite = 0

Branch = 1

RegDst = X

ALUSrc = 0

MemtoReg = X

X indicates the signal is not used (don't care)

# Step 5: Implementing Control


- Truth table based on instruction analysis

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	0110
1	X	X	X	0	0	0	0	0010
1	X	X	X	0	0	1	0	0110
1	X	X	X	0	1	0	0	0000
1	X	X	X	0	1	0	1	0001
1	X	X	X	1	0	1	0	0111


Fig 4.13 The truth table for the 4 ALU control bits (called Operation).
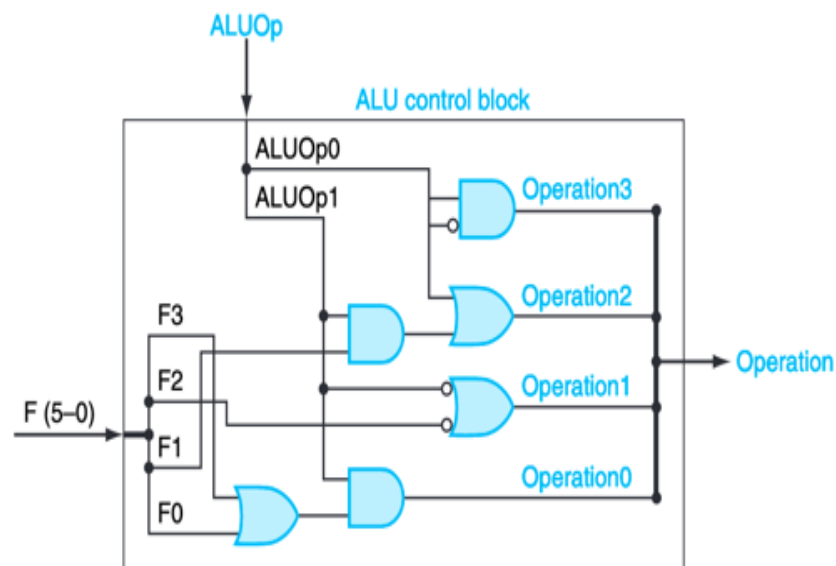
# Step 5: Implementing Control

- Simple combinational logic based on truth tables




ALU Control Unit

 


Main Control Unit

# Implementing Jumps

 


- Jump uses word address
- Need one more option (more datapath elements) to update PC as concatenation of
  - Top 4 bits of old PC
  - 26-bit jump address
  - 00
- Need an extra control signal decoded from opcode to choose which one to use

# Datapath With Jumps Added

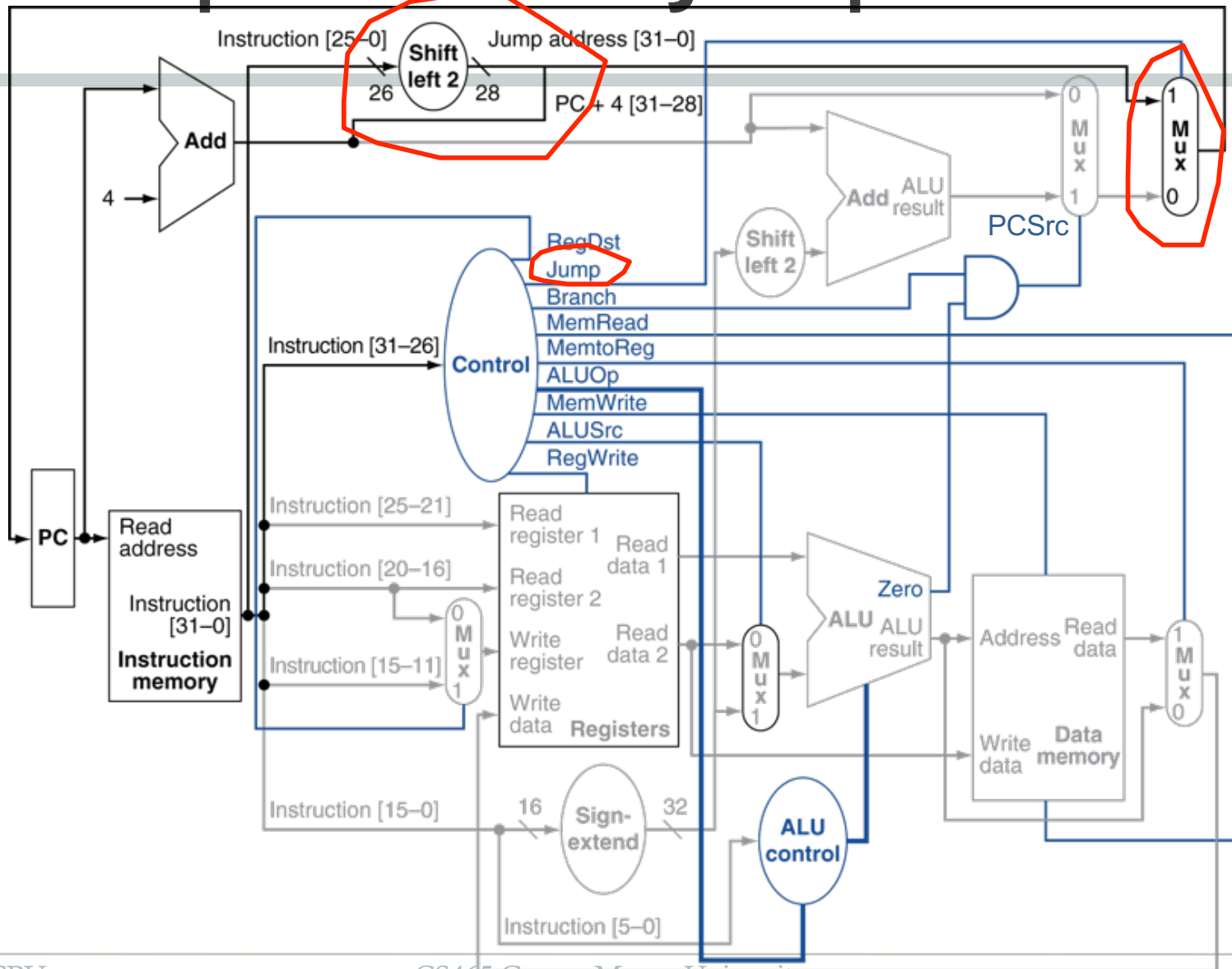




# Complete Single Cycle Processor

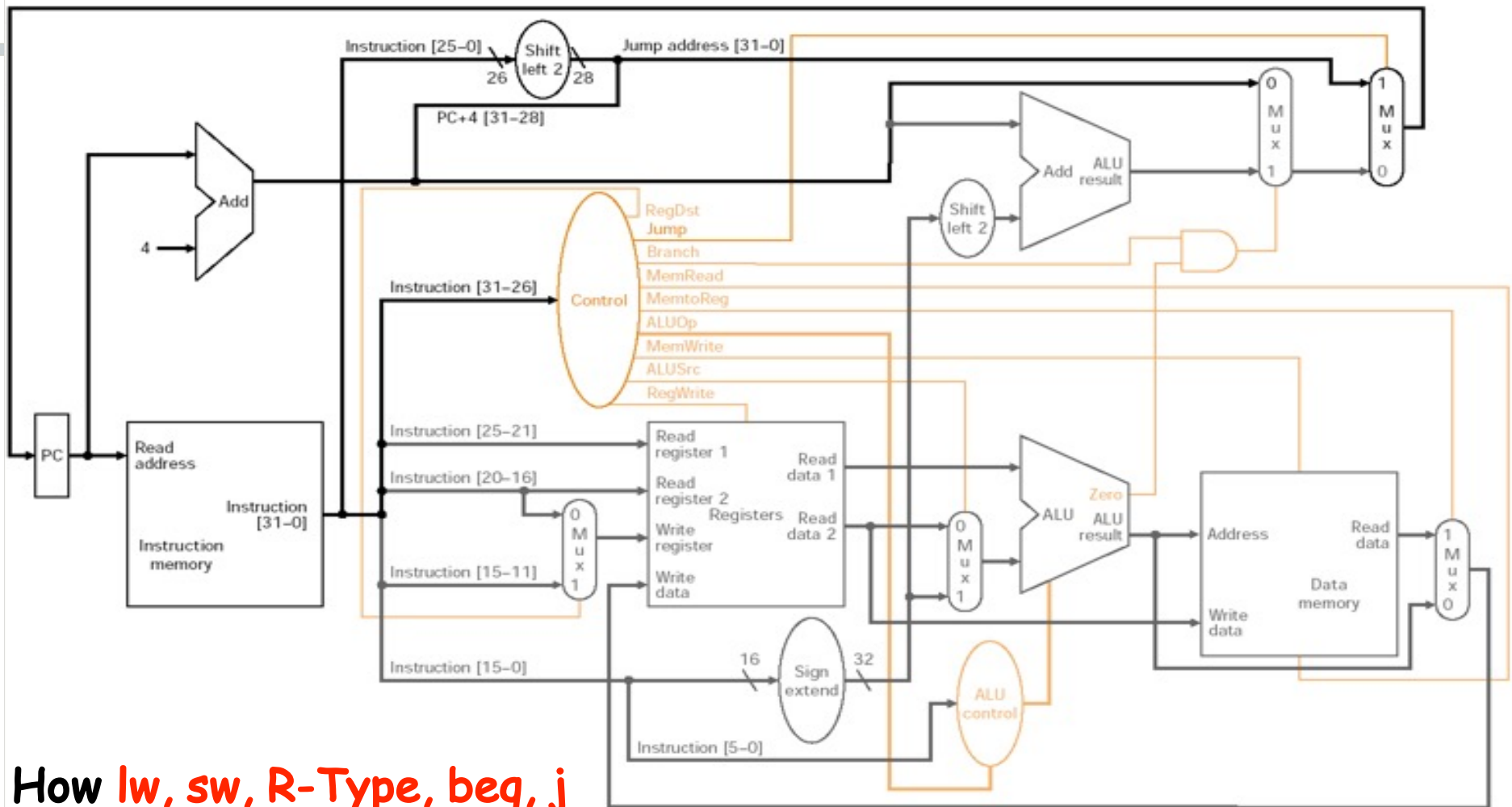


How **lw**, **sw**, **R-Type**, **beq**, **j** instructions work?

# Delays in Single Cycle Datapath

 


What are the delays for **lw, sw, R-Type, beq, j** instructions?

# Delays in Single Cycle Datapath

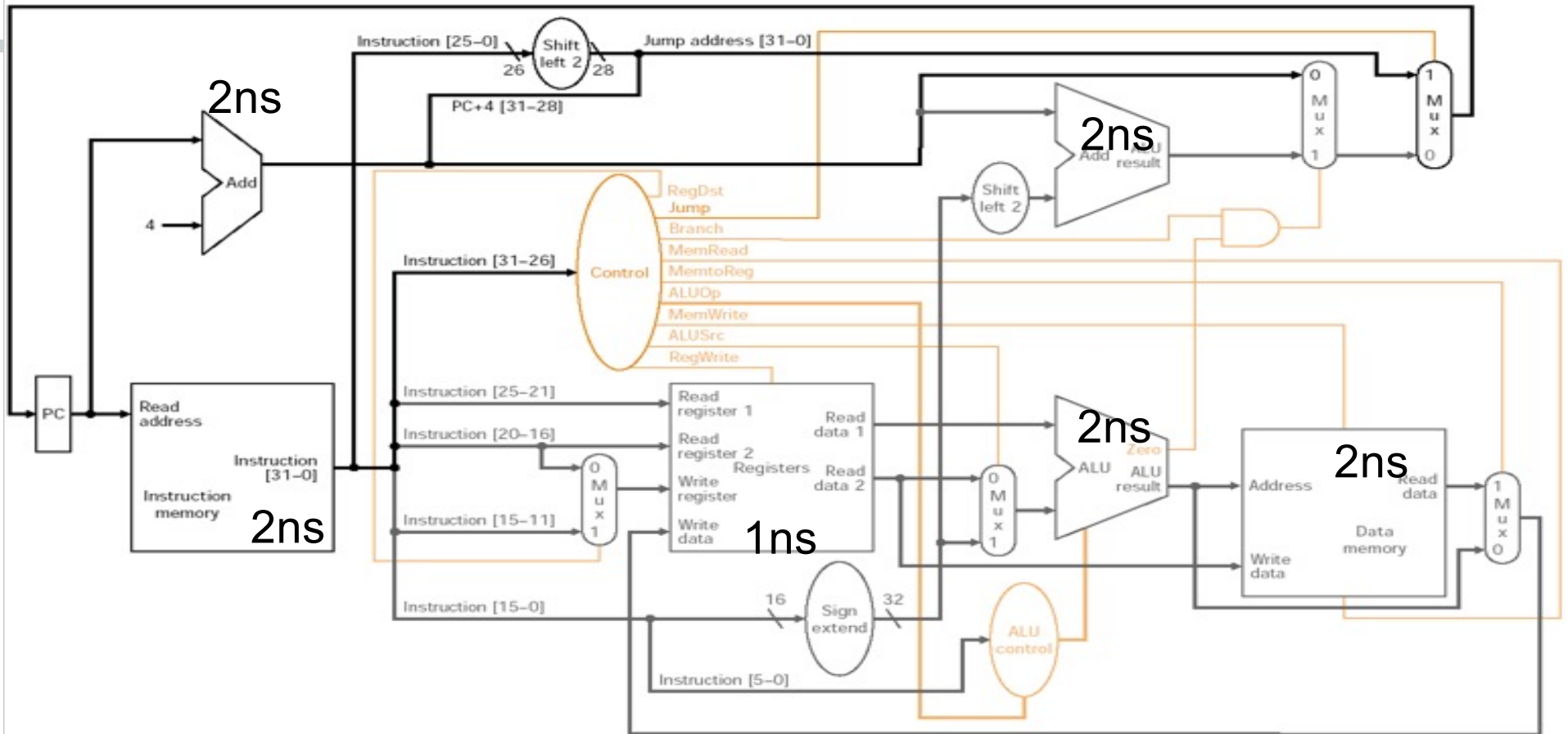


What is the delay for an **R-Type** instruction?

# Delays in Single Cycle Datapath

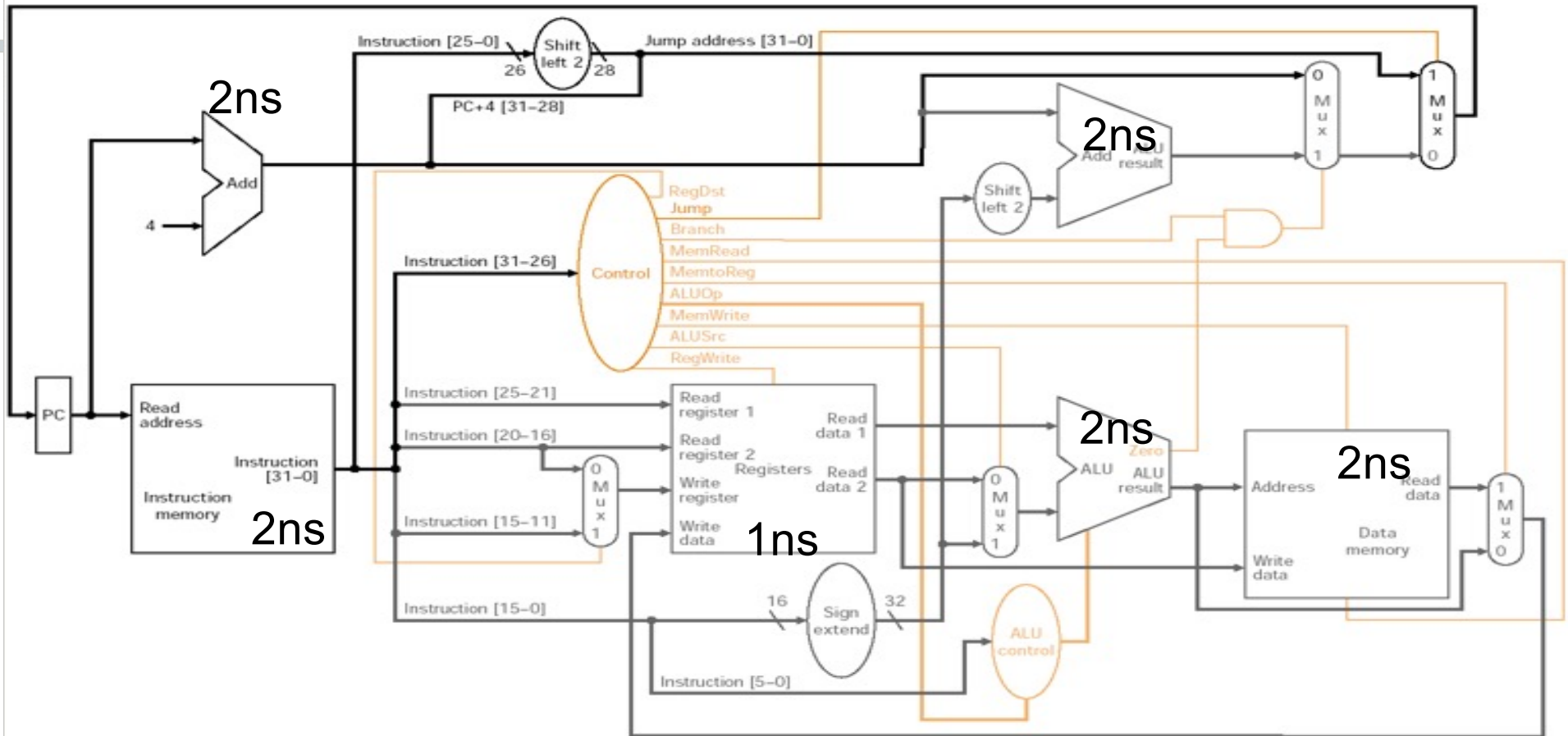

What is the delay for a **beq** instruction?

# Delays in Single Cycle Datapath

 

What is the delay for a **lw** instruction?

# Delay in Single Cycle Datapath

- Calculate by assuming negligible delays except:
  - memory (2ns), ALU and adders (2ns), register file access (1ns)

Instruction class	Instruction Fetch (Memory)	Register Access	ALU	Memory Access	Register Access	
R-Type	X	X	X		X	6
Load	X	X	X	X	X	8
Store	X	X	X	X		7
Branch	X	X	X			5
Jump	X					2

# Performance Issues

- Single cycle datapath  $\Rightarrow$  CPI=1, Clock Cycle Time  $\Rightarrow$  long
- Longest delay determines clock period
  - Critical path: load instruction
    - Instruction memory  $\rightarrow$  register file  $\rightarrow$  ALU  $\rightarrow$  data memory  $\rightarrow$  (register file)
- Violates design principle
  - Making the common case fast
- We will improve performance by pipelining



# Summary

- 5 steps to design a processor
  - 1. Analyze instruction set => datapath requirements
  - 2. Select set of datapath components & establish clock methodology
  - 3. Assemble datapath meeting the requirements
  - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer
  - 5. Assemble the control logic
- MIPS makes it easier
  - Instructions same size
  - Source registers always in same place
  - Immediates same size, location
  - Operations always on registers/immediates