

CS465: Computer Systems Architecture

Lecture 5: Arithmetic for Computers


*Slides adapted from Computer Organization and Design by
Patterson and Henessey

Outline

- Operations on integers
 - Addition and subtraction (check review material; Ch3.2)
 - Multiplication and division
 - Dealing with overflow
- Floating-point numbers
 - Representation (check review material; Ch 3.5)
 - Addition and multiplication

Example: Integer Addition

- Example: $7 + 6$

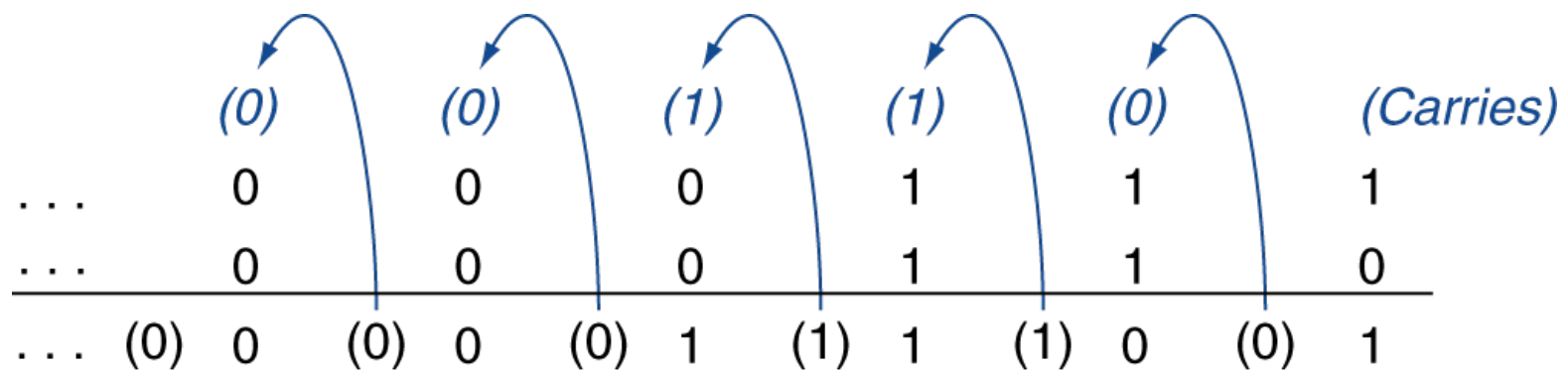

When Overflow Occurs ?


- Overflow if result out of range
- For unsigned integers:
 - Adding has a carry from MSB
- For signed integers:
 - Adding +ve and -ve operands, no overflow
 - Adding two +ve operands
 - Overflow if result sign is 1
 - Adding two -ve operands
 - Overflow if result sign is 0

Dealing with Overflow

- MIPS unsigned integer arithmetic instructions ignore overflow:
 - `addu, addui, subu`
 - Useful for C unsigned integers
- MIPS signed integer arithmetic instructions trigger an exception on overflow
 - `add, addi, sub`
 - Useful for languages that require raising an exception (e.g., Ada, Fortran)
 - On overflow, invoke exception handler
 - Save PC in exception program counter (EPC) register
 - Jump to predefined handler address
 - `mfc0` (move from coprocessor 0 reg) instruction can retrieve EPC value, to return after corrective action

Review: Boolean Algebra & Gates

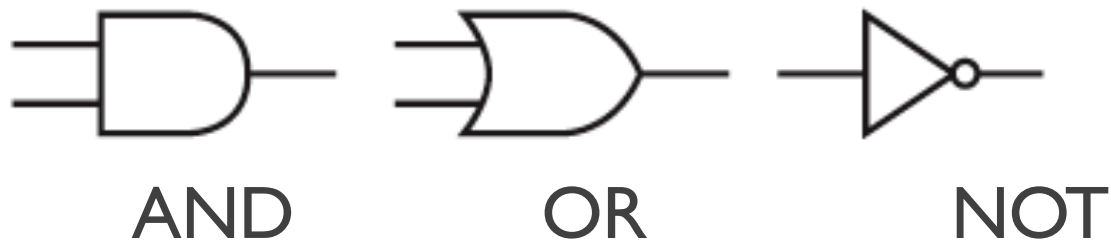
- Basic operations
 - AND, OR, NOT
- Complicated operations
 - XOR, NOR, NAND
- Logic gates



- See details in Appendix B of textbook

Review: Multiplexor

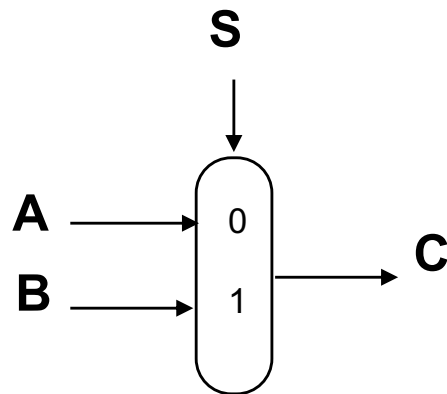- Selects one of the inputs to be the output, based on a control input






Note: we call this a 2-input mux even though it has 3 inputs!

- MUX is needed for building **ALU**
 - **A**rithmetic **L**ogic **U**nit: a digital circuit that performs Arithmetic (Add, Sub, ...) and Logical (AND, OR, NOT) operations

1-bit Adder

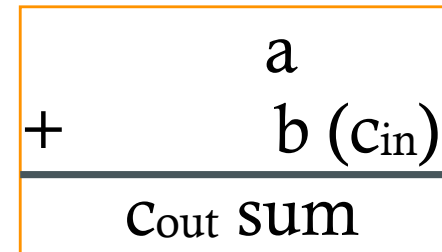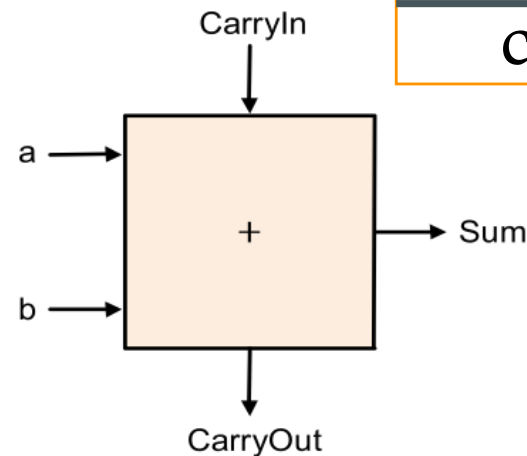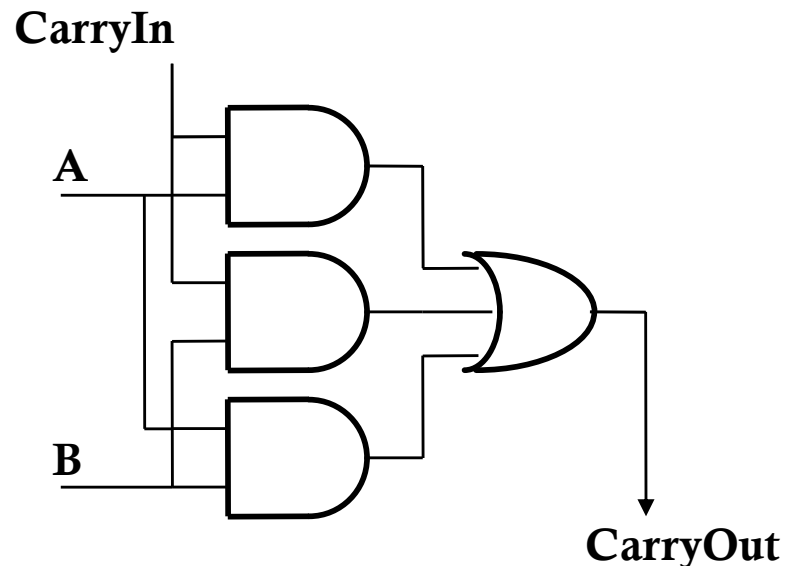
- 1-bit addition generates two result bits
 - $c_{out} = (a \text{ and } b) \text{ or } (a \text{ and } c_{in}) \text{ or } (b \text{ and } c_{in})$
 - $sum = a \text{ xor } b \text{ xor } c_{in}$



(3, 2) adder


1-bit ALU

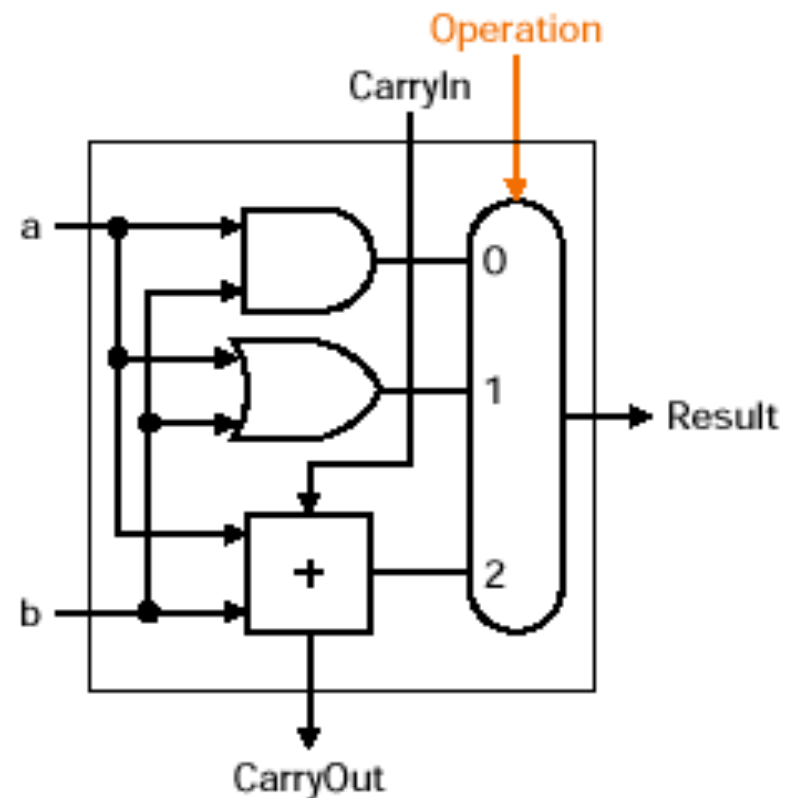- Design trick: take pieces you know and try to put them together
 - Multiplexor
- A 1-bit ALU that performs AND, OR, and addition



What about Subtraction?

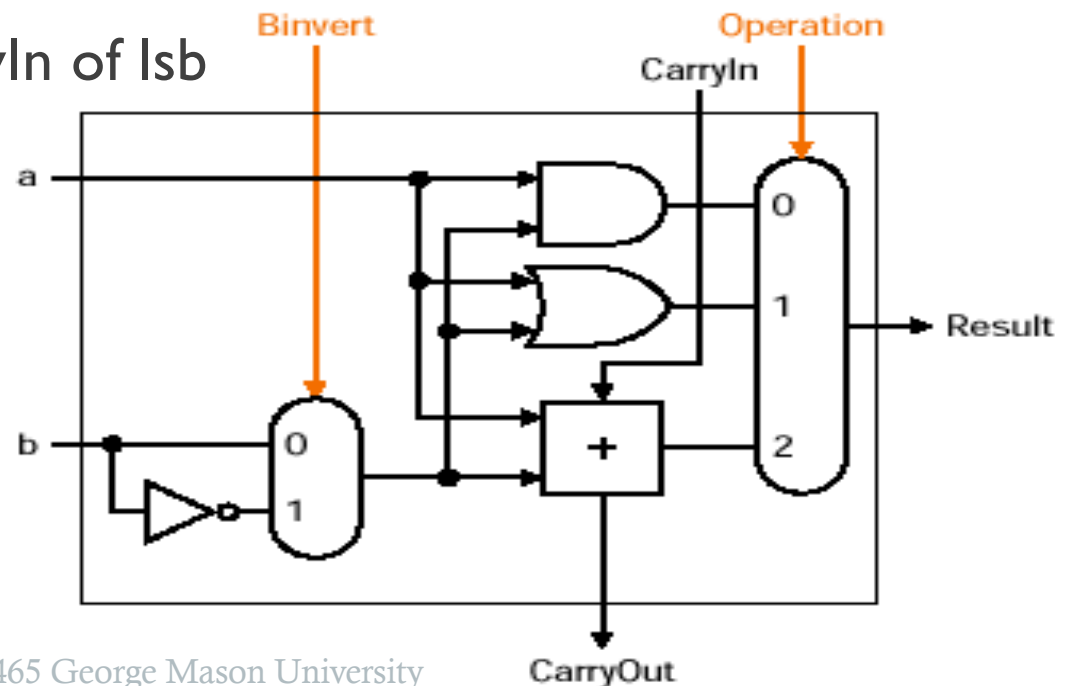- Remember $a - b = a + (-b)$
 - Two's complement of $(-b)$: invert each bit (by inverter) of b and add 1 at lsb
- How do we implement?
 - Bit invert: simple
 - “Add 1”: set the CarryIn of lsb




Expanding ALU

- Expanding data length
 - By paralleling the one-bit ALUs and some other modification on the logical circuits, we can create bigger ALUs
- Expanding functionality for MIPS
 - `slt $t0, $s1, $s2`
 - Idea: set \$t0 according to the sign bit of (\$s1-\$s2)
 - `beq $s1,$s2,label`
 - Idea: or all the bits of (\$s1-\$s2) for zero checking

32-bit ALU for MIPS

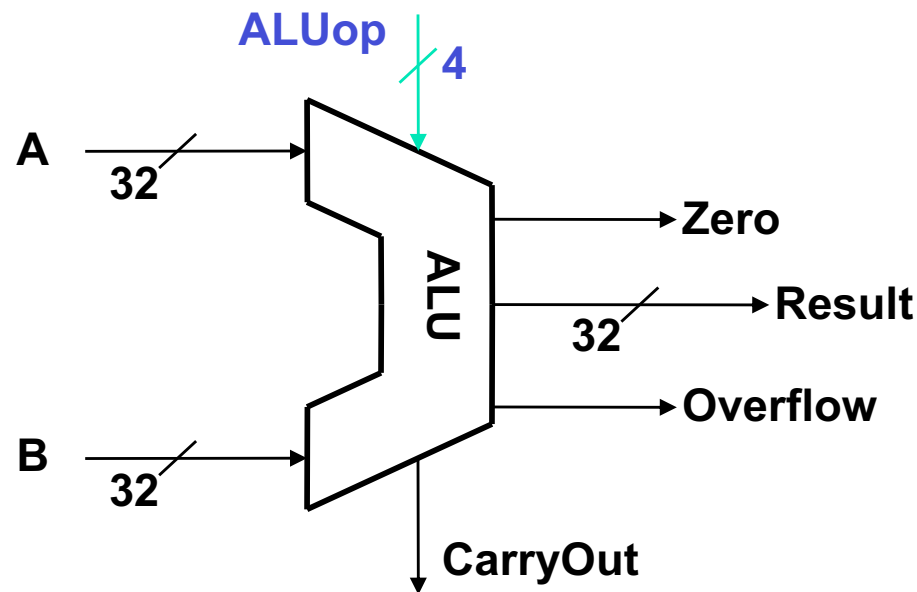- Operations supported: and, or, nor, add, sub, slt, beq/bne
- See Appendix B for details



Roadmap

- Operations on integers
 - Addition and subtraction
 - Multiplication
 - Division
- Floating-point numbers
 - Representation
 - Addition and multiplication